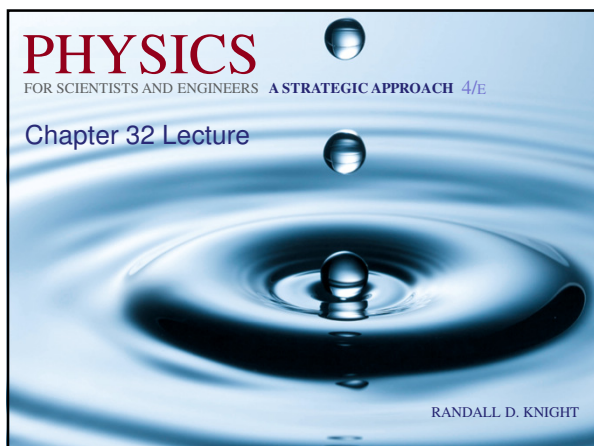



PHYSICS
 FOR SCIENTISTS AND ENGINEERS A STRATEGIC APPROACH 4/E

Chapter 32 Lecture



RANDALL D. KNIGHT

Chapter 32 AC Circuits

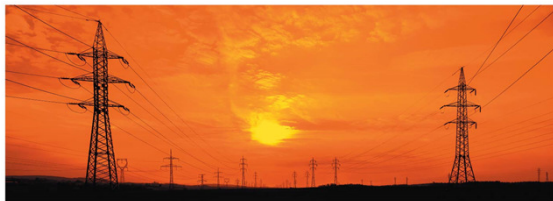


IN THIS CHAPTER, you will learn about and analyze AC circuits.

© 2017 Pearson Education, Inc. Slide 32-2

Chapter 32 Preview

What is an AC circuit?

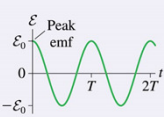The circuits of Chapter 28, with a steady current in one direction, are called **DC circuits**—*direct current*. A circuit with an oscillating emf is called an **AC circuit**, for *alternating current*. The wires that transport electricity across the country—the grid—use alternating current.



« LOOKING BACK Chapter 28 Circuits


© 2017 Pearson Education, Inc. Slide 32-3

Chapter 32 Preview

How do circuit elements act in an AC circuit?

Resistors in an AC circuit act as they do in a DC circuit. But you'll learn that capacitors and inductors are more useful in AC circuits than in DC circuits.

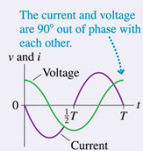- The voltage across and the current through a capacitor or inductor are **90° out of phase**. One is peaking when the other is zero, and vice versa.
- The **peak voltage** V and **peak current** I have an Ohm's-law-like relationship $V = IX$, where X , which depends on frequency, is called the **reactance**.
- Unlike resistors, capacitors and inductors **do not dissipate energy**.



◀ LOOKING BACK Section 26.5 Capacitors
 ◀ LOOKING BACK Section 30.8 Inductors


© 2017 Pearson Education, Inc.

Slide 32-4

Chapter 32 Preview

What is a phasor?

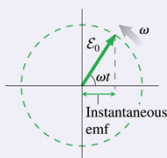AC voltages **oscillate sinusoidally**, so the mathematics of AC circuits is that of SHM. You'll learn a new way to represent oscillating quantities—as a rotating vector called a **phasor**. The instantaneous value of a phasor quantity is its horizontal projection.



◀ LOOKING BACK Chapter 15 Simple harmonic motion and resonance


© 2017 Pearson Education, Inc.

Slide 32-5

Chapter 32 Preview

What is an RLC circuit?

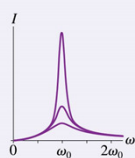A circuit with a resistor, inductor, and capacitor in series is called an **RLC circuit**. An **RLC circuit** has a **resonance**—a large current over a narrow range of frequencies—that allows it to be tuned to a specific frequency. As a result, **RLC circuits** are very important in communications.



© 2017 Pearson Education, Inc.

Slide 32-6

Chapter 32 Preview

Why are AC circuits important?

AC circuits are the backbone of our technological society. **Generators** automatically produce an oscillating emf, AC power is easily transported over large distances, and **transformers** allow engineers to shift the AC voltage up or down. The circuits of radio, television, and **cell phones** are also AC circuits because they work with oscillating voltages and currents—at much higher frequencies than the grid, but the physical principles are the same.

© 2017 Pearson Education, Inc.

Slide 32-7

Chapter 32 Reading Questions

Chapter 32 Reading Questions

© 2017 Pearson Education, Inc.

Slide 32-8

Reading Question 32.1

In Chapter 32, “AC” stands for

- A. Air cooling.
- B. Air conditioning.
- C. All current.
- D. Alternating current.
- E. Analog current.

© 2017 Pearson Education, Inc.

Slide 32-9

Reading Question 32.1

In Chapter 32, "AC" stands for

- A. Air cooling.
- B. Air conditioning.
- C. All current.
- D. Alternating current.
- E. Analog current.

© 2017 Pearson Education, Inc.

Slide 32-10

Reading Question 32.2

The analysis of AC circuits uses a rotating vector called a

- A. Rotor.
- B. Wiggler.
- C. Phasor.
- D. Motor.
- E. Variator.

© 2017 Pearson Education, Inc.

Slide 32-11

Reading Question 32.2

The analysis of AC circuits uses a rotating vector called a

- A. Rotor.
- B. Wiggler.
- C. Phasor.
- D. Motor.
- E. Variator.

© 2017 Pearson Education, Inc.

Slide 32-12

Reading Question 32.3

In a capacitor, the peak current and peak voltage are related by the

- A. Capacitive resistance.
- B. Capacitive reactance.
- C. Capacitive impedance.
- D. Capacitive inductance.

© 2017 Pearson Education, Inc.

Slide 32-13

Reading Question 32.3

In a capacitor, the peak current and peak voltage are related by the

- A. Capacitive resistance.
- B. **Capacitive reactance.**
- C. Capacitive impedance.
- D. Capacitive inductance.

© 2017 Pearson Education, Inc.

Slide 32-14

Reading Question 32.4

In a series *RLC* circuit, what quantity is maximum at resonance?

- A. The voltage
- B. The current
- C. The impedance
- D. The phase

© 2017 Pearson Education, Inc.

Slide 32-15

Reading Question 32.4

In a series *RLC* circuit, what quantity is maximum at resonance?

- A. The voltage
- B. The current
- C. The impedance
- D. The phase

© 2017 Pearson Education, Inc.

Slide 32-16

Reading Question 32.5

In the United States a typical electrical outlet has a "line voltage" of 120 V. This is actually the

- A. Average voltage.
- B. Maximum voltage.
- C. Maximum voltage minus the minimum voltage.
- D. Minimum voltage.
- E. rms voltage.

© 2017 Pearson Education, Inc.

Slide 32-17

Reading Question 32.5

In the United States a typical electrical outlet has a "line voltage" of 120 V. This is actually the

- A. Average voltage.
- B. Maximum voltage.
- C. Maximum voltage minus the minimum voltage.
- D. Minimum voltage.
- E. rms voltage.


© 2017 Pearson Education, Inc.

Slide 32-18

Chapter 32 Content, Examples, and QuickCheck Questions

© 2017 Pearson Education, Inc. Slide 32-19

AC Sources and Phasors

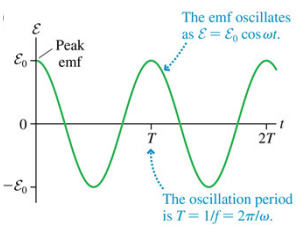

The emf oscillates as $\mathcal{E} = \mathcal{E}_0 \cos \omega t$.


The oscillation period is $T = 1/f = 2\pi/\omega$.

- Circuits powered by a sinusoidal emf are called **AC circuits**, where AC stands for *alternating current*.
- Steady-current circuits studied in Chapter 28 are called DC circuits, for *direct current*.
- The instantaneous emf of an AC generator or oscillator can be written

$$\mathcal{E} = \mathcal{E}_0 \cos \omega t$$

© 2017 Pearson Education, Inc. Slide 32-20

AC Sources and Phasors

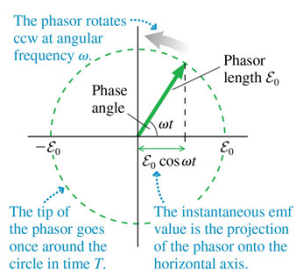


- An alternative way to represent the emf and other oscillatory quantities is with a *phasor diagram*, as shown.
- A **phasor** is a vector that rotates *counterclockwise* (ccw) around the origin at angular frequency ω .
- The quantity's value at time t is the projection of the phasor onto the horizontal axis.

© 2017 Pearson Education, Inc. Slide 32-21

AC Sources and Phasors

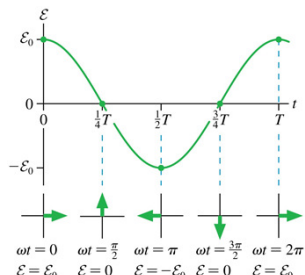- The figure below helps you visualize the phasor rotation by showing how the phasor corresponds to the more familiar graph at several specific points in the cycle.




© 2017 Pearson Education, Inc.

Slide 32-22

QuickCheck 32.1

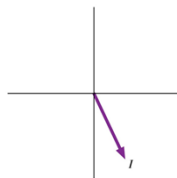This is a current phasor. The magnitude of the instantaneous value of the current is




- A. Increasing.
- B. Decreasing.
- C. Constant.
- D. Can't tell without knowing which way it is rotating.

© 2017 Pearson Education, Inc.

Slide 32-23

QuickCheck 32.1

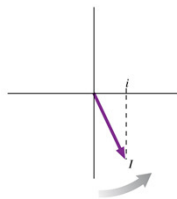This is a current phasor. The magnitude of the instantaneous value of the current is




- A. Increasing.
- B. Decreasing.
- C. Constant.
- D. Can't tell without knowing which way it is rotating.

© 2017 Pearson Education, Inc.

Slide 32-24

Resistor Circuits

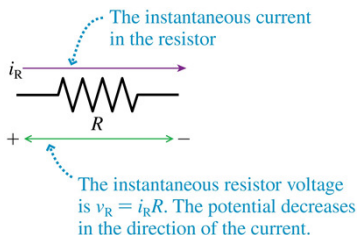- In Chapter 28 we used the symbols I and V for DC current and voltage.
- Now, because the current and voltage are oscillating, we will use lowercase i to represent the instantaneous current and v for the instantaneous voltage.




© 2017 Pearson Education, Inc.

Slide 32-25

Resistor Circuits

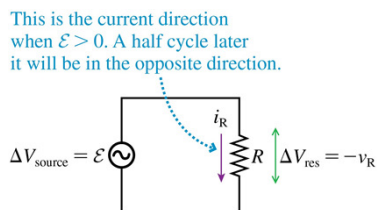- The figure shows a resistor R connected across an AC generator of peak emf equal to V_R .



- The current through the resistor is

$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$


where $I_R = V_R/R$ is the peak current.

© 2017 Pearson Education, Inc.

Slide 32-26

Resistor Circuits

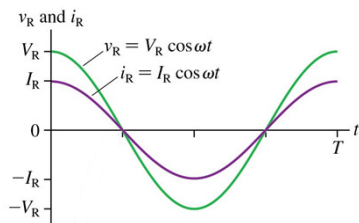- The resistor's instantaneous current and voltage are *in phase*, both oscillating as $\cos \omega t$.




$$i_R = \frac{v_R}{R} = \frac{V_R \cos \omega t}{R} = I_R \cos \omega t$$

© 2017 Pearson Education, Inc.

Slide 32-27

Resistor Circuits

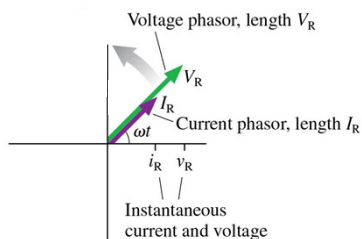
- Below is the phasor diagram for the resistor circuit.
- V_R and I_R point in the same direction, indicating that resistor voltage and current oscillate in phase.



© 2017 Pearson Education, Inc. Slide 32-28

Capacitor Circuits

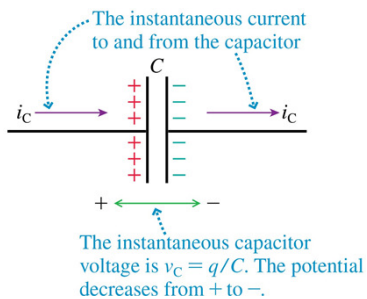
- The figure shows current i_C charging a capacitor with capacitance C .



© 2017 Pearson Education, Inc. Slide 32-29

Capacitor Circuits

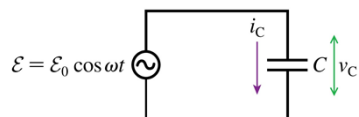- The figure shows a capacitor C connected across an AC generator of peak emf equal to V_C .



- The charge sitting on the positive plate of the capacitor at a particular instant is

$$q = C v_C = C V_C \cos \omega t$$

© 2017 Pearson Education, Inc. Slide 32-30

Capacitor Circuits

- The current is the rate at which charge flows through the wires, $i_C = dq/dt$, thus

$$i_C = \frac{dq}{dt} = \frac{d}{dt}(CV_C \cos \omega t) = -\omega CV_C \sin \omega t$$
- We can most easily see the relationship between the capacitor voltage and current if we use the trigonometric identity

$$-\sin(x) = \cos(x + \pi/2)$$
 to write

$$i_C = \omega CV_C \cos\left(\omega t + \frac{\pi}{2}\right)$$

© 2017 Pearson Education, Inc. Slide 32-31

Capacitor Circuits

- A capacitor's current and voltage are *not* in phase.
- The current peaks one-quarter of a period *before* the voltage peaks.

$$i_C = \omega CV_C \cos\left(\omega t + \frac{\pi}{2}\right)$$

© 2017 Pearson Education, Inc. Slide 32-32


Capacitor Circuits

- Below is the phasor diagram for the capacitor circuit.
- The AC current of a capacitor *leads* the capacitor voltage by $\pi/2$ rad, or 90° .

© 2017 Pearson Education, Inc. Slide 32-33

QuickCheck 32.2

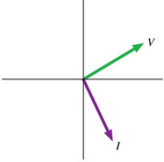In the circuit represented by these phasors, the current ____ the voltage




- A. leads
- B. lags
- C. is perpendicular to
- D. is out of phase with

© 2017 Pearson Education, Inc. Slide 32-34

QuickCheck 32.2

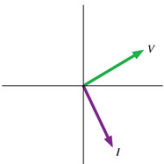In the circuit represented by these phasors, the current ____ the voltage




- A. leads
- B. lags
- C. is perpendicular to
- D. is out of phase with

© 2017 Pearson Education, Inc. Slide 32-35

QuickCheck 32.3

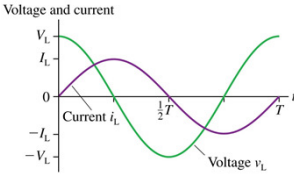In the circuit represented by these graphs, the current ____ the voltage




- A. leads
- B. lags
- C. is less than
- D. is out of phase with

© 2017 Pearson Education, Inc. Slide 32-36

QuickCheck 32.3

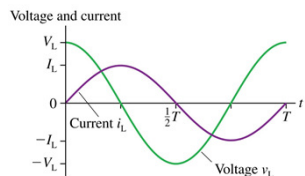In the circuit represented by these graphs, the current _____ the voltage




- A. leads
- B. lags
- C. is less than
- D. is out of phase with

© 2017 Pearson Education, Inc. Slide 32-37

Capacitive Reactance

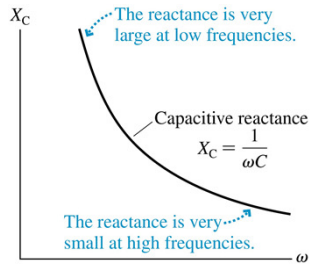- The peak current to and from a capacitor is $I_C = \omega C V_C$.
- We can find a relationship that looks similar to Ohm's Law if we define the **capacitive reactance** to be




$$X_C \equiv \frac{1}{\omega C}$$

$$I_C = \frac{V_C}{X_C} \text{ or } V_C = I_C X_C$$

© 2017 Pearson Education, Inc. Slide 32-38

QuickCheck 32.4

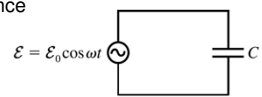If the value of the capacitance is doubled, the capacitive reactance




- A. Is quartered.
- B. Is halved.
- C. Is doubled.
- D. Is quadrupled.
- E. Can't tell without knowing ω .

© 2017 Pearson Education, Inc. Slide 32-39

QuickCheck 32.4

If the value of the capacitance is doubled, the capacitive reactance

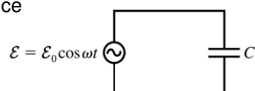- A. Is quartered.
 ✓ B. **Is halved.** $X_C = \frac{1}{\omega C}$
 C. Is doubled.
 D. Is quadrupled.
 E. Can't tell without knowing ω .




© 2017 Pearson Education, Inc.

Slide 32-40

QuickCheck 32.5

If the value of the capacitance is doubled, the peak current

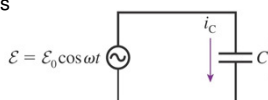- A. Is quartered.
 B. Is halved.
 C. Is doubled.
 D. Is quadrupled.
 E. Can't tell without knowing C .




© 2017 Pearson Education, Inc.

Slide 32-41

QuickCheck 32.5

If the value of the capacitance is doubled, the peak current

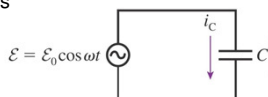- A. Is quartered.
 B. Is halved.
 ✓ C. **Is doubled.** $I_C = \frac{V_C}{X_C} = \frac{\mathcal{E}}{X_C}$
 D. Is quadrupled.
 E. Can't tell without knowing C .



© 2017 Pearson Education, Inc.

Slide 32-42

Example 32.2 Capacitive Reactance

EXAMPLE 32.2 Capacitive reactance

What is the capacitive reactance of a $0.10 \mu\text{F}$ capacitor at 100 Hz (an audio frequency) and at 100 MHz (an FM-radio frequency)?

SOLVE At 100 Hz,

$$X_C(\text{at } 100 \text{ Hz}) = \frac{1}{\omega C} = \frac{1}{2\pi(100 \text{ Hz})(1.0 \times 10^{-7} \text{ F})} = 16,000 \Omega$$

Increasing the frequency by a factor of 10^6 decreases X_C by a factor of 10^6 , giving

$$X_C(\text{at } 100 \text{ MHz}) = 0.016 \Omega$$

ASSESS A capacitor with a substantial reactance at audio frequencies has virtually no reactance at FM-radio frequencies.

© 2017 Pearson Education, Inc.


Slide 32-43

Example 32.3 Capacitor Current

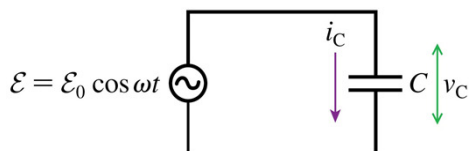EXAMPLE 32.3 Capacitor current

A $10 \mu\text{F}$ capacitor is connected to a 1000 Hz oscillator with a peak emf of 5.0 V. What is the peak current to the capacitor?

VISUALIZE Figure 32.7b showed the circuit diagram. It is a simple one-capacitor circuit.



© 2017 Pearson Education, Inc.

Slide 32-44

Example 32.3 Capacitor Current

EXAMPLE 32.3 Capacitor current

SOLVE The capacitive reactance at $\omega = 2\pi f = 6280 \text{ rad/s}$ is

$$X_C = \frac{1}{\omega C} = \frac{1}{(6280 \text{ rad/s})(10 \times 10^{-6} \text{ F})} = 16 \Omega$$

The peak voltage across the capacitor is $V_C = \mathcal{E}_0 = 5.0 \text{ V}$; hence the peak current is


$$I_C = \frac{V_C}{X_C} = \frac{5.0 \text{ V}}{16 \Omega} = 0.31 \text{ A}$$

ASSESS Using reactance is just like using Ohm's law, but don't forget it applies to only the *peak* current and voltage, not the instantaneous values.

© 2017 Pearson Education, Inc.

Slide 32-45

RC Filter Circuits

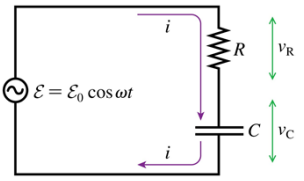


The figure shows a circuit in which a resistor R and capacitor C are in series with an emf oscillating at angular frequency ω .

- If the frequency is very low, the capacitive reactance will be very large, and thus the peak current I_C will be very small.
- If the frequency is very high, the capacitive reactance approaches zero and the peak current, determined by the resistance alone, will be $I_R = \mathcal{E}_0/R$.

© 2017 Pearson Education, Inc. Slide 32-46

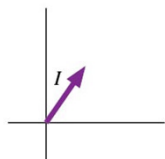
Using Phasors to Analyze an RC Circuit Step 1 of 4



- Begin by drawing a current phasor of length I .
- This is the starting point because the series circuit elements have the same current i .
- The angle at which the phasor is drawn is not relevant.

© 2017 Pearson Education, Inc. Slide 32-47

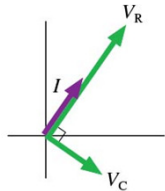
Using Phasors to Analyze an RC Circuit Step 2 of 4



- The current and voltage of a resistor are in phase, so draw a resistor voltage phasor of length V_R parallel to the current phasor I .
- The capacitor current leads the capacitor voltage by 90° , so draw a capacitor voltage phasor of length V_C that is 90° behind the current phasor.

© 2017 Pearson Education, Inc. Slide 32-48

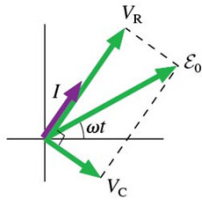
Using Phasors to Analyze an RC Circuit
Step 3 of 4



- The series resistor and capacitor are in parallel with the emf, so their *instantaneous* voltages satisfy $v_R + v_C = \mathcal{E}$.
- This is a *vector* addition of phasors.
- The emf is $\mathcal{E} = \mathcal{E}_0 \cos \omega t$, hence the emf phasor is at angle ωt .

© 2017 Pearson Education, Inc. Slide 32-49

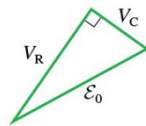Using Phasors to Analyze an RC Circuit
Step 4 of 4



- The length of the emf phasor, \mathcal{E}_0 , is the hypotenuse of a right triangle formed by the resistor and capacitor phasors.
- Thus $\mathcal{E}_0^2 = V_R^2 + V_C^2$

© 2017 Pearson Education, Inc. Slide 32-50

RC Filter Circuits

- The relationship $\mathcal{E}_0^2 = V_R^2 + V_C^2$ is based on the peak values.
- The peak voltages are related to the peak current by $V_R = IR$ and $V_C = IX_C$, so

$$\begin{aligned} \mathcal{E}_0^2 &= V_R^2 + V_C^2 = (IR)^2 + (IX_C)^2 = (R^2 + X_C^2)I^2 \\ &= (R^2 + 1/\omega^2 C^2)I^2 \end{aligned}$$

- This can be solved for the peak current, which in turn gives us the two peak voltages:

$$V_R = IR = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + X_C^2}} = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + 1/\omega^2 C^2}}$$


$$V_C = IX_C = \frac{\mathcal{E}_0 X_C}{\sqrt{R^2 + X_C^2}} = \frac{\mathcal{E}_0 / \omega C}{\sqrt{R^2 + 1/\omega^2 C^2}}$$

© 2017 Pearson Education, Inc. Slide 32-51

RC Filter Circuits

- The figure shows a graph of the resistor and capacitor peak voltages as functions of the emf angular frequency ω .
- The frequency at which $V_R = V_C$ is called the **crossover frequency**:

$$\omega_c = \frac{1}{RC}$$

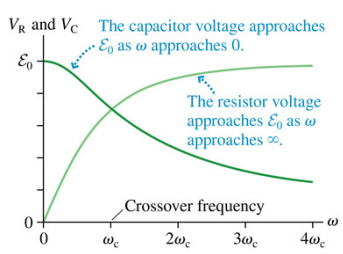


© 2017 Pearson Education, Inc. Slide 32-52

QuickCheck 32.6

Does $V_R + V_C = \mathcal{E}_0$?

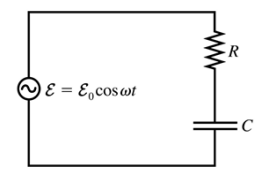A. Yes
B. No.
C. Can't tell without knowing ω .




© 2017 Pearson Education, Inc. Slide 32-53

QuickCheck 32.6

Does $V_R + V_C = \mathcal{E}_0$?

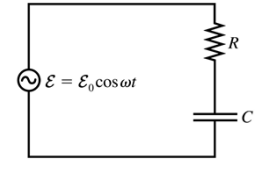A. Yes
B. No
C. Can't tell without knowing ω .

Instantaneous voltages add.
Peak voltages don't because the voltages are not in phase.



© 2017 Pearson Education, Inc. Slide 32-54

RC Filter Circuits

- The figure below shows an RC circuit in which v_C is the *output voltage*.
- This circuit is called a **low-pass filter**.

© 2017 Pearson Education, Inc. Slide 32-55

RC Filter Circuits

- The figure below shows an RC circuit in which v_R is the *output voltage*.
- This circuit is called a **high-pass filter**.

© 2017 Pearson Education, Inc. Slide 32-56

Inductor Circuits

- The figure shows the instantaneous current i_L through an inductor.
- If the current is *changing*, the instantaneous inductor voltage is


$$v_L = L \frac{di_L}{dt}$$

- The potential decreases in the direction of the current if the current is increasing, and increases if the current is decreasing.

© 2017 Pearson Education, Inc. Slide 32-57

Inductor Circuits

- The figure shows an inductor L connected across an AC generator of peak emf equal to V_L .

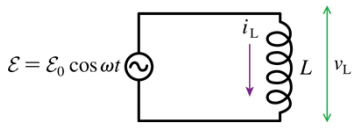$\mathcal{E} = \mathcal{E}_0 \cos \omega t$


- The instantaneous inductor voltage is equal to the emf:

$$v_L = V_L \cos \omega t$$

© 2017 Pearson Education, Inc. Slide 32-58

Inductor Circuits

- Combining the two previous equations for v_L gives

$$di_L = \frac{v_L}{L} dt = \frac{V_L}{L} \cos \omega t dt$$

- Integrating gives

$$i_L = \frac{V_L}{L} \int \cos \omega t dt = \frac{V_L}{\omega L} \sin \omega t = \frac{V_L}{\omega L} \cos \left(\omega t - \frac{\pi}{2} \right)$$


$$= I_L \cos \left(\omega t - \frac{\pi}{2} \right)$$

where $I_L = V_L / \omega L$ is the peak or maximum inductor current.

© 2017 Pearson Education, Inc. Slide 32-59

Inductor Circuits

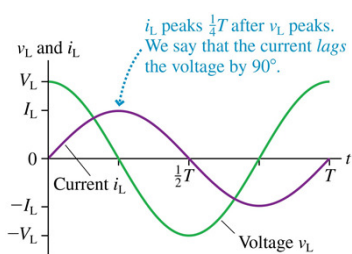- An inductor's current and voltage are *not* in phase.
- The current peaks one-quarter of a period after the voltage peaks.




$$i_L = I_L \cos \left(\omega t - \frac{\pi}{2} \right)$$

© 2017 Pearson Education, Inc. Slide 32-60

Inductor Circuits

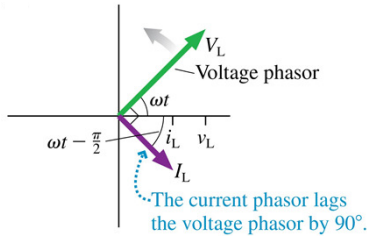- Below is the phasor diagram for the inductor circuit.
- The AC current through an inductor *lags* the inductor voltage by $\pi/2$ rad, or 90° .




© 2017 Pearson Education, Inc. Slide 32-61

Inductive Reactance

- We define the **inductive reactance**, analogous to the capacitive reactance, to be

$$X_L \equiv \omega L$$

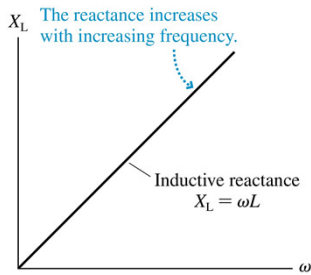

$$I_L = \frac{V_L}{X_L} \text{ or } V_L = I_L X_L$$

© 2017 Pearson Education, Inc. Slide 32-62

Example 32.5 Current and Voltage of an Inductor

EXAMPLE 32.5 Current and voltage of an inductor

A $25 \mu\text{H}$ inductor is used in a circuit that oscillates at 100 kHz . The current through the inductor reaches a peak value of 20 mA at $t = 5.0 \mu\text{s}$. What is the peak inductor voltage, and when, closest to $t = 5.0 \mu\text{s}$, does it occur?


MODEL The inductor current lags the voltage by 90° , or, equivalently, the voltage reaches its peak value one-quarter period *before* the current.

© 2017 Pearson Education, Inc. Slide 32-63

Example 32.5 Current and Voltage of an Inductor

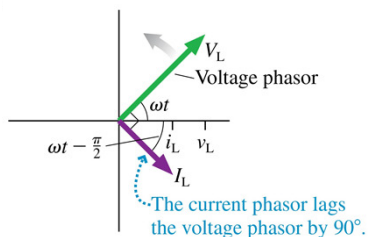EXAMPLE 32.5 Current and voltage of an inductor

VISUALIZE The circuit looks like Figure 32.15b.



© 2017 Pearson Education, Inc.

Slide 32-64

Example 32.5 Current and Voltage of an Inductor

EXAMPLE 32.5 Current and voltage of an inductor

SOLVE The inductive reactance at $f = 100$ kHz is

$$X_L = \omega L = 2\pi(1.0 \times 10^5 \text{ Hz})(25 \times 10^{-6} \text{ H}) = 16 \Omega$$


Thus the peak voltage is $V_L = I_L X_L = (20 \text{ mA})(16 \Omega) = 320 \text{ mV}$. The voltage peak occurs one-quarter period before the current peaks, and we know that the current peaks at $t = 5.0 \mu\text{s}$. The period of a 100 kHz oscillation is $10.0 \mu\text{s}$, so the voltage peaks at

$$t = 5.0 \mu\text{s} - \frac{10.0 \mu\text{s}}{4} = 2.5 \mu\text{s}$$

© 2017 Pearson Education, Inc.

Slide 32-65

The Series RLC Circuit

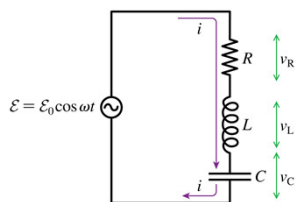


▪ The circuit shown, where a resistor, inductor, and capacitor are in series, is called a series RLC circuit.

- The instantaneous current of all three elements is the same: $i = i_R = i_L = i_C$
- The sum of the instantaneous voltages matches the emf: $\mathcal{E} = v_R + v_L + v_C$

© 2017 Pearson Education, Inc.

Slide 32-66

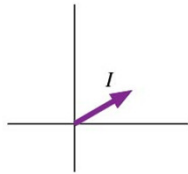Using Phasors to Analyze an *RLC* Circuit
Step 1 of 4




- Begin by drawing a current phasor of length I .
- This is the starting point because the series circuit elements have the same current I .
- The angle at which the phasor is drawn is not relevant.

© 2017 Pearson Education, Inc.

Slide 32-67

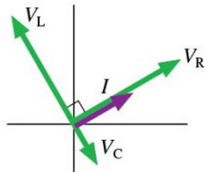Using Phasors to Analyze an *RLC* Circuit
Step 2 of 4




- The current and voltage of a resistor are in phase, so draw a resistor voltage phasor parallel to the current phasor I .
- The capacitor current *leads* the capacitor voltage, so draw a capacitor voltage phasor that is 90° behind the current phasor.
- The inductor current *lags* the voltage, so draw an inductor voltage phasor that is 90° ahead of the current phasor.

© 2017 Pearson Education, Inc.

Slide 32-68

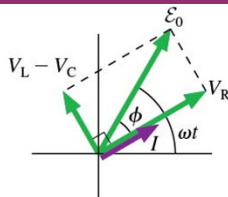Using Phasors to Analyze an *RLC* Circuit
Step 3 of 4




- The *instantaneous* voltages satisfy $\mathcal{E} = v_R + v_L + v_C$.
- This is a *vector* addition of phasors.
- Because the capacitor and inductor phasors are in opposite directions, their vector sum has length $V_L - V_C$.
- Adding the resistor phasor, at right angles, then gives the emf phasor \mathcal{E} at angle ωt .

© 2017 Pearson Education, Inc.

Slide 32-69

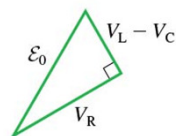Using Phasors to Analyze an *RLC* Circuit Step 4 of 4



- The length of the emf phasor, \mathcal{E}_0 , is the hypotenuse of a right triangle.
- Thus $\mathcal{E}_0^2 = V_R^2 + (V_L - V_C)^2$

© 2017 Pearson Education, Inc.

Slide 32-70

The Series *RLC* Circuit

- If $V_L < V_C$, which we've assumed, then the instantaneous current i lags the emf by a phase angle ϕ :

$$i = I \cos(\omega t - \phi)$$

- Based on the right-triangle, the square of the peak voltage is

$$\mathcal{E}_0^2 = V_R^2 + (V_L - V_C)^2 = [R^2 + (X_L - X_C)^2]I^2$$

where we wrote each of the peak voltages in terms of the peak current I and a resistance or a reactance.

- Consequently, the peak current in the *RLC* circuit is


$$I = \frac{\mathcal{E}_0}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{\mathcal{E}_0}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$

© 2017 Pearson Education, Inc.

Slide 32-71

Phase Angle in a Series *RLC* Circuit

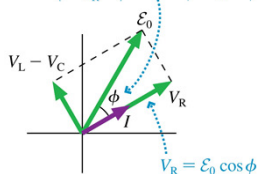The current lags the emf by
 $\phi = \tan^{-1} \left(\frac{V_L - V_C}{V_R} \right) = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$




- It is often useful to know the phase angle ϕ between the emf and the current in an *RLC* circuit:

$$\phi = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$

© 2017 Pearson Education, Inc.

Slide 32-72

Resonance in a Series RLC Circuit

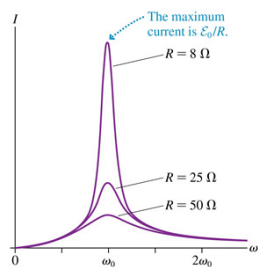

- Suppose we vary the emf frequency ω while keeping everything else constant.
- There is very little current at very low or very high frequencies.
- I is maximum when $X_L = X_C$, which occurs at the **resonance frequency**:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


© 2017 Pearson Education, Inc.

Slide 32-73

QuickCheck 32.7

If the value of R is increased, the resonance frequency of this circuit

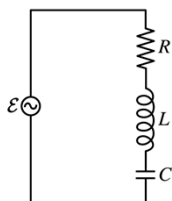- A. Increases.
- B. Decreases.
- C. Stays the same.



© 2017 Pearson Education, Inc.


Slide 32-74

QuickCheck 32.7

If the value of R is increased, the resonance frequency of this circuit

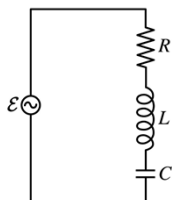- A. Increases.
- B. Decreases.
- C. Stays the same.

The resonance frequency depends on C and L but not on R .




© 2017 Pearson Education, Inc.

Slide 32-75

QuickCheck 32.8

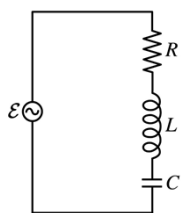The resonance frequency of this circuit is 1000 Hz. To change the resonance frequency to 2000 Hz, replace the capacitor with one having capacitance




- A. $C/4$
- B. $C/2$
- C. $2C$
- D. $4C$
- E. It's impossible to change the resonance frequency by changing only the capacitor.

© 2017 Pearson Education, Inc. Slide 32-76

QuickCheck 32.8

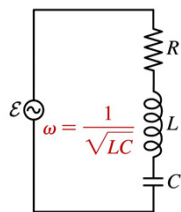The resonance frequency of this circuit is 1000 Hz. To change the resonance frequency to 2000 Hz, replace the capacitor with one having capacitance




- A. $C/4$
- B. $C/2$
- C. $2C$
- D. $4C$
- E. It's impossible to change the resonance frequency by changing only the capacitor.

© 2017 Pearson Education, Inc. Slide 32-77

Resonance in a Series RLC Circuit

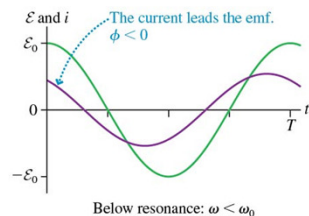- Below is a graph of the instantaneous emf and current in a series RLC circuit driven *below* the resonance frequency: $\omega < \omega_0$
- In this case, $X_L < X_C$, and ϕ is negative.



© 2017 Pearson Education, Inc. Slide 32-78

Resonance in a Series RLC Circuit

- Below is a graph of the instantaneous emf and current in a series RLC circuit driven at the resonance frequency: $\omega = \omega_0$
- In this case, $X_L = X_C$, and $\phi = 0$

© 2017 Pearson Education, Inc. Slide 32-79

Resonance in a Series RLC Circuit

- Below is a graph of the instantaneous emf and current in a series RLC circuit driven above the resonance frequency: $\omega > \omega_0$
- In this case, $X_L > X_C$, and ϕ is positive.

© 2017 Pearson Education, Inc. Slide 32-80

Power in AC Circuits

- The graphs show the instantaneous power loss in a resistor R carrying a current i_R :

$$p_R = i_R^2 R = I_R^2 R \cos^2 \omega t$$
- The average power P_R is the total energy dissipated per second:

$$P_R = \frac{1}{2} I_R^2 R \quad (\text{average power loss in a resistor})$$

© 2017 Pearson Education, Inc. Slide 32-81

Power in AC Circuits

- We can define the **root-mean-square** current and voltage as

$$I_{\text{rms}} = \frac{I_R}{\sqrt{2}} \quad V_{\text{rms}} = \frac{V_R}{\sqrt{2}}$$

- The resistor's average power loss in terms of the rms quantities is

$$P_R = (I_{\text{rms}})^2 R = \frac{(V_{\text{rms}})^2}{R} = I_{\text{rms}} V_{\text{rms}}$$



The power rating on a lightbulb is its average power at $V_{\text{rms}} = 120 \text{ V}$.

- The average power supplied by the emf is

$$P_{\text{source}} = I_{\text{rms}} \mathcal{E}_{\text{rms}}$$

© 2017 Pearson Education, Inc.

Slide 32-82


Example 32.7 Lighting a Bulb

EXAMPLE 32.7 Lighting a bulb

A 100 W incandescent lightbulb is plugged into a 120 V/60 Hz outlet. What is the resistance of the bulb's filament? What is the peak current through the bulb?

MODEL The filament in a lightbulb acts as a resistor.

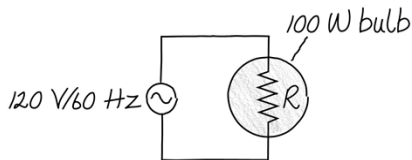VISUALIZE FIGURE 32.21 is a simple one-resistor circuit.



© 2017 Pearson Education, Inc.

Slide 32-83

Example 32.7 Lighting a Bulb

EXAMPLE 32.7 Lighting a bulb

SOLVE A bulb labeled 100 W is designed to dissipate an average 100 W at $V_{\text{rms}} = 120 \text{ V}$. We can use Equation 32.39 to find

$$R = \frac{(V_{\text{rms}})^2}{P_R} = \frac{(120 \text{ V})^2}{100 \text{ W}} = 144 \Omega$$

The rms current is then found from

$$I_{\text{rms}} = \frac{P_R}{V_{\text{rms}}} = \frac{100 \text{ W}}{120 \text{ V}} = 0.833 \text{ A}$$


The peak current is $I_R = \sqrt{2} I_{\text{rms}} = 1.18 \text{ A}$.

ASSESS Calculations with rms values are just like the calculations for DC circuits.

© 2017 Pearson Education, Inc.

Slide 32-84

Capacitors in AC Circuits

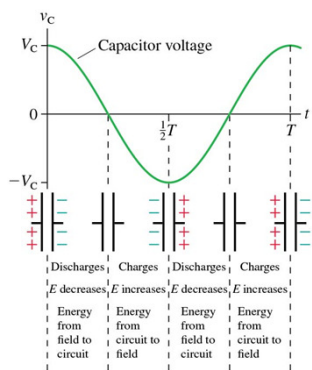


- Energy flows into and out of a capacitor as it is charged and discharged.
- The energy is not dissipated, as it would be by a resistor.
- The energy is stored as potential energy in the capacitor's electric field.

© 2017 Pearson Education, Inc. Slide 32-85

Capacitors in AC Circuits

- The instantaneous power flowing into a capacitor is

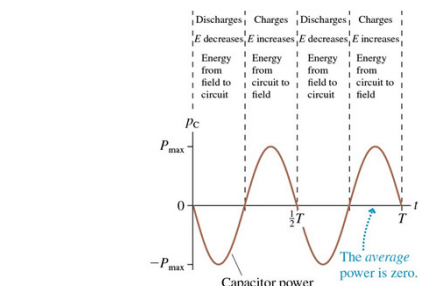
$$p_C = v_C i_C = (V_C \cos \omega t)(- \omega C V_C \sin \omega t) = -\frac{1}{2} \omega C V_C^2 \sin 2\omega t$$


© 2017 Pearson Education, Inc. Slide 32-86

The Power Factor in RLC Circuits

- In an RLC circuit, energy is supplied by the emf and dissipated by the resistor.
- The average power supplied by the emf is:

$$P_{\text{source}} = \frac{1}{2} I E_0 \cos \phi = I_{\text{rms}} \mathcal{E}_{\text{rms}} \cos \phi$$
- The term $\cos \phi$, called the **power factor**, arises because the current and the emf are not in phase.
- Large industrial motors, such as the one shown, operate most efficiently, doing the maximum work per second, when the power factor is as close to 1 as possible.



© 2017 Pearson Education, Inc. Slide 32-87

Chapter 32 Summary Slides

© 2017 Pearson Education, Inc. Slide 32-88

Important Concepts

AC circuits are driven by an emf
 $\mathcal{E} = \mathcal{E}_0 \cos \omega t$
 that oscillates with angular frequency $\omega = 2\pi f$.

Phasors can be used to represent the oscillating emf, current, and voltage.

© 2017 Pearson Education, Inc. Slide 32-89

Important Concepts

Basic circuit elements				
Element	i and v	Resistance/ reactance	I and V	Power
Resistor	In phase	R is fixed	$V = IR$	$I_{\text{rms}} V_{\text{rms}}$
Capacitor	i leads v by 90°	$X_C = 1/\omega C$	$V = IX_C$	0
Inductor	i lags v by 90°	$X_L = \omega L$	$V = IX_L$	0

For many purposes, especially calculating power, the **root-mean-square (rms)** quantities

$$V_{\text{rms}} = V/\sqrt{2} \quad I_{\text{rms}} = I/\sqrt{2} \quad \mathcal{E}_{\text{rms}} = \mathcal{E}_0/\sqrt{2}$$

are equivalent to the corresponding DC quantities.

© 2017 Pearson Education, Inc. Slide 32-90

Key Skills

Using phasor diagrams

- Start with a phasor (v or i) common to two or more circuit elements.
- The sum of instantaneous quantities is vector addition.
- Use the Pythagorean theorem to relate peak quantities.



For an RC circuit, shown here,

$$v_R + v_C = \mathcal{E}$$

$$V_R^2 + V_C^2 = \mathcal{E}_0^2$$

© 2017 Pearson Education, Inc.

Slide 32-91

Key Skills

Instantaneous and peak quantities

The instantaneous quantities v and i vary sinusoidally. The peak quantities V and I are the maximum values of v and i . For capacitors and inductors, the peak quantities are related by $V = IX$, where X is the reactance, but this relationship does *not* apply to v and i .

Kirchhoff's loop law says that the sum of the potential differences around a loop is zero.


Charge conservation says that circuit elements in series all have the same instantaneous current i and the same peak current I .

© 2017 Pearson Education, Inc.

Slide 32-92

Applications


RC filter circuits

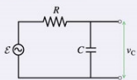

$$v_C = \frac{\mathcal{E}_0 X_C}{\sqrt{R^2 + X_C^2}}$$

$$v_C \rightarrow \mathcal{E}_0 \text{ as } \omega \rightarrow 0$$

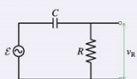A **low-pass filter** transmits low frequencies and blocks high frequencies.



$$v_R = \frac{\mathcal{E}_0 R}{\sqrt{R^2 + X_C^2}}$$

$$v_R \rightarrow \mathcal{E}_0 \text{ as } \omega \rightarrow \infty$$


A **high-pass filter** transmits high frequencies and blocks low frequencies.

© 2017 Pearson Education, Inc.

Slide 32-93

Applications

Series RLC circuits

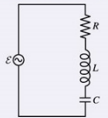

$I = \mathcal{E}_0/Z$ where Z is the impedance

$Z = \sqrt{R^2 + (X_L - X_C)^2}$

$V_R = IR \quad V_L = IX_L \quad V_C = IX_C$

When $\omega = \omega_0 = 1/\sqrt{LC}$ (the resonance frequency), the current in the circuit is a maximum $I_{\max} = \mathcal{E}_0/R$.

In general, the current i lags behind \mathcal{E} by the phase angle $\phi = \tan^{-1}((X_L - X_C)/R)$.

The power supplied by the emf is $P_{\text{source}} = I_{\text{rms}} \mathcal{E}_{\text{rms}} \cos \phi$, where $\cos \phi$ is called the power factor.

The power lost in the resistor is $P_R = I_{\text{rms}} V_{\text{rms}} = (I_{\text{rms}})^2 R$.

© 2017 Pearson Education, Inc.

Slide 32-94
